



移动通信工程学院

School of Mobile Information Engineering

中山大學
SUN YAT-SEN UNIVERSITY

Single Cycle Processor Design

Kai Huang





Rise of the robots

The Economist

Mar 29th 2014

Workers of the world

 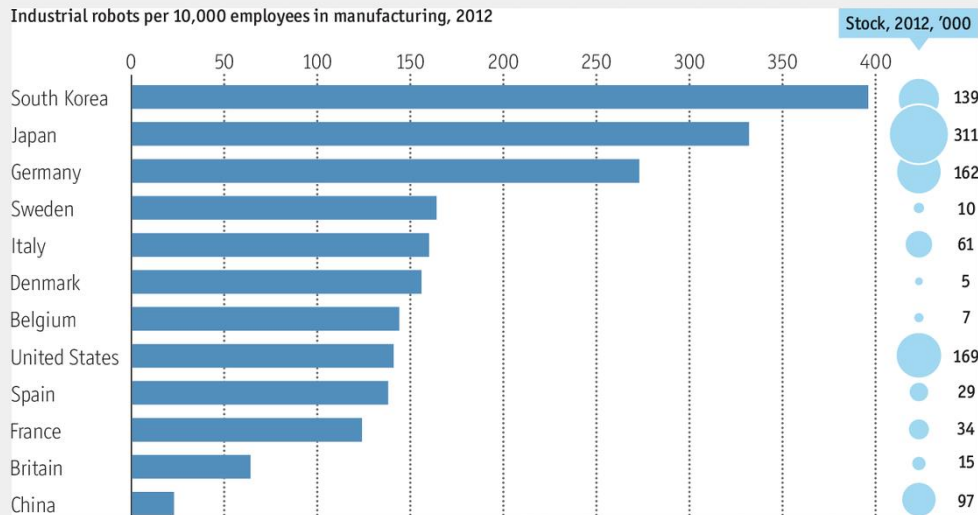

Source: World Robotics 2013

<http://www.economist.com/printedition/2014-03-29>



移动信息工程学院

School of Mobile Information Engineering

4/4/2014

Kai.Huang@SYSU

2

中山大学
SUN YAT-SEN UNIVERSITY




Outline

- Designing a Processor: Step-by-Step
- Datapath Components and Clocking
- Assembling an Adequate Datapath
- Controlling the Execution of Instructions
- The Main Controller and ALU Controller
- Drawback of the single-cycle processor design

The Performance Perspective

 - Recall, performance is determined by:
 - Instruction count
 - Clock cycles per instruction (CPI)
 - Clock cycle time (CT)
- Processor design will affect
 - Clock cycles per instruction
 - Clock cycle time
- Single cycle datapath and control design:
 - Advantage: One clock cycle per instruction
 - Disadvantage: long cycle time






Designing a Processor: Step-by-Step

- Analyze instruction set => **datapath requirements**
 - The meaning of each instruction is given by the **register transfers**
 - Datapath must include storage elements for ISA registers
 - Datapath must support each register transfer
- Select **datapath components** and **clocking methodology**
- Assemble **datapath** meeting the requirements
- Analyze implementation of **each instruction**
 - Determine the setting of **control signals** for register transfer
- Assemble the **control logic**

MIPS Instruction Formats

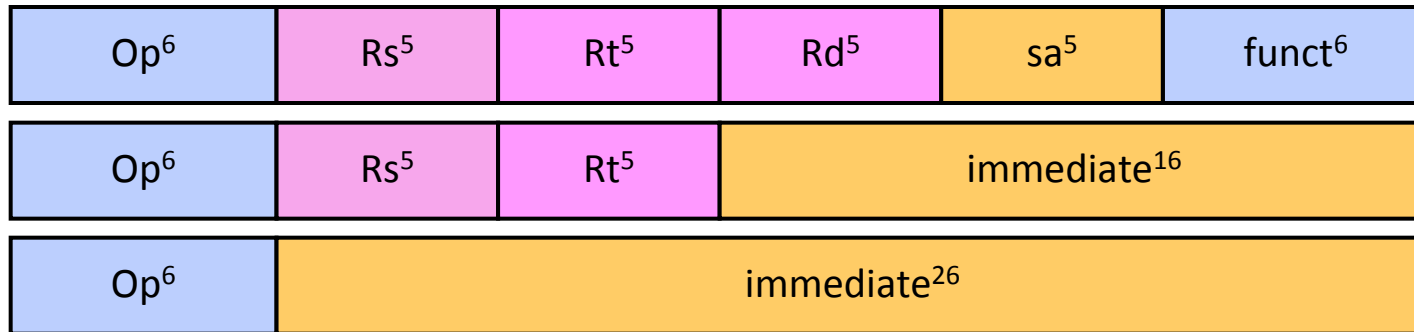- All instructions are **32-bit wide**
- Three instruction formats: **R-type**, **I-type**, and **J-type**



- Op⁶: 6-bit opcode of the instruction
- Rs⁵, Rt⁵, Rd⁵: 5-bit source and destination register numbers
- sa⁵: 5-bit shift amount used by shift instructions
- funct⁶: 6-bit function field for R-type instructions
- immediate¹⁶: 16-bit immediate value or address offset
- immediate²⁶: 26-bit target address of the jump instruction

MIPS Subset of Instructions

- Only a subset of the MIPS instructions are considered
 - ALU instructions (R-type): **add, sub, and, or, xor, slt**
 - Immediate instructions (I-type): **addi, slti, andi, ori, xori**
 - Load and Store (I-type): **lw, sw**
 - Branch (I-type): **beq, bne**
 - Jump (J-type): **j**
- This subset does not include all the integer instructions
- But sufficient to illustrate design of datapath and control
- Concepts used to implement the MIPS subset are used to construct a broad spectrum of computers

Details of the MIPS Subset

Instruction		Meaning	Format					
add	rd, rs, rt	addition	$op^6 = 0$	rs^5	rt^5	rd^5	0	0x20
sub	rd, rs, rt	subtraction	$op^6 = 0$	rs^5	rt^5	rd^5	0	0x22
and	rd, rs, rt	bitwise and	$op^6 = 0$	rs^5	rt^5	rd^5	0	0x24
or	rd, rs, rt	bitwise or	$op^6 = 0$	rs^5	rt^5	rd^5	0	0x25
xor	rd, rs, rt	exclusive or	$op^6 = 0$	rs^5	rt^5	rd^5	0	0x26
slt	rd, rs, rt	set on less than	$op^6 = 0$	rs^5	rt^5	rd^5	0	0x2a
addi	rt, rs, im^{16}	add immediate	0x08	rs^5	rt^5	im^{16}		
slti	rt, rs, im^{16}	slt immediate	0x0a	rs^5	rt^5	im^{16}		
andi	rt, rs, im^{16}	and immediate	0x0c	rs^5	rt^5	im^{16}		
ori	rt, rs, im^{16}	or immediate	0x0d	rs^5	rt^5	im^{16}		
xori	rt, im^{16}	xor immediate	0x0e	rs^5	rt^5	im^{16}		
lw	rt, $im^{16}(rs)$	load word	0x23	rs^5	rt^5	im^{16}		
sw	rt, $im^{16}(rs)$	store word	0x2b	rs^5	rt^5	im^{16}		
beq	rs, rt, im^{16}	branch if equal	0x04	rs^5	rt^5	im^{16}		
bne	rs, rt, im^{16}	branch not equal	0x05	rs^5	rt^5	im^{16}		
j	im^{26}	jump	0x02	im^{26}				

Register Transfer Level (RTL)

- RTL is a description of data flow between registers
- RTL gives a **meaning** to the instructions
- All instructions are fetched from memory at address PC

Instruction RTL Description

ADD	$\text{Reg(Rd)} \leftarrow \text{Reg(Rs)} + \text{Reg(Rt)};$	$\text{PC} \leftarrow \text{PC} + 4$
SUB	$\text{Reg(Rd)} \leftarrow \text{Reg(Rs)} - \text{Reg(Rt)};$	$\text{PC} \leftarrow \text{PC} + 4$
ORI	$\text{Reg(Rt)} \leftarrow \text{Reg(Rs)} \mid \text{zero_ext(Im16)};$	$\text{PC} \leftarrow \text{PC} + 4$
LW	$\text{Reg(Rt)} \leftarrow \text{MEM}[\text{Reg(Rs)} + \text{sign_ext(Im16)}];$	$\text{PC} \leftarrow \text{PC} + 4$
SW	$\text{MEM}[\text{Reg(Rs)} + \text{sign_ext(Im16)}] \leftarrow \text{Reg(Rt)};$	$\text{PC} \leftarrow \text{PC} + 4$
BEQ	$\text{if (Reg(Rs) == Reg(Rt))}$ $\text{PC} \leftarrow \text{PC} + 4 + 4 \times \text{sign_extend(Im16)}$ else $\text{PC} \leftarrow \text{PC} + 4$	

Instructions are Executed in Steps

- **R-type**
 - Fetch instruction: $\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
 - Fetch operands: $\text{data1} \leftarrow \text{Reg}(\text{Rs}), \text{data2} \leftarrow \text{Reg}(\text{Rt})$
 - Execute operation: $\text{ALU_result} \leftarrow \text{func}(\text{data1}, \text{data2})$
 - Write ALU result: $\text{Reg}(\text{Rd}) \leftarrow \text{ALU_result}$
 - Next PC address: $\text{PC} \leftarrow \text{PC} + 4$
- **I-type**
 - Fetch instruction: $\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
 - Fetch operands: $\text{data1} \leftarrow \text{Reg}(\text{Rs}), \text{data2} \leftarrow \text{Extend}(\text{imm16})$
 - Execute operation: $\text{ALU_result} \leftarrow \text{op}(\text{data1}, \text{data2})$
 - Write ALU result: $\text{Reg}(\text{Rt}) \leftarrow \text{ALU_result}$
 - Next PC address: $\text{PC} \leftarrow \text{PC} + 4$
- **BEQ**
 - Fetch instruction: $\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
 - Fetch operands: $\text{data1} \leftarrow \text{Reg}(\text{Rs}), \text{data2} \leftarrow \text{Reg}(\text{Rt})$
 - Equality: $\text{zero} \leftarrow \text{subtract}(\text{data1}, \text{data2})$
 - Branch: $\text{if (zero) } \text{PC} \leftarrow \text{PC} + 4 + 4 \times \text{sign_ext}(\text{imm16})$
else $\text{PC} \leftarrow \text{PC} + 4$



Instruction Execution – cont'd

- **LW**
 - Fetch instruction: $\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
 - Fetch base register: $\text{base} \leftarrow \text{Reg}(\text{Rs})$
 - Calculate address: $\text{address} \leftarrow \text{base} + \text{sign_extend}(\text{imm16})$
 - Read memory: $\text{data} \leftarrow \text{MEM}[\text{address}]$
 - Write register Rt: $\text{Reg}(\text{Rt}) \leftarrow \text{data}$
 - Next PC address: $\text{PC} \leftarrow \text{PC} + 4$

- **SW**
 - Fetch instruction: $\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
 - Fetch registers: $\text{base} \leftarrow \text{Reg}(\text{Rs}), \text{data} \leftarrow \text{Reg}(\text{Rt})$
 - Calculate address: $\text{address} \leftarrow \text{base} + \text{sign_extend}(\text{imm16})$
 - Write memory: $\text{MEM}[\text{address}] \leftarrow \text{data}$
 - Next PC address: $\text{PC} \leftarrow \text{PC} + 4$

- **Jump**
 - Fetch instruction: $\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
 - Target PC address: $\text{target} \leftarrow \text{PC}[31:28], \text{Imm26}, \text{'00'}$
 - Jump: $\text{PC} \leftarrow \text{target}$

concatenation

Requirements of the Instruction Set

- Memory
 - **Instruction memory** where instructions are stored
 - **Data memory** where data is stored
- Registers
 - **32 × 32-bit general purpose registers**, R0 is always zero
 - Read source register Rs
 - Read source register Rt
 - Write destination register Rt or Rd
- Program counter **PC register** and **Adder** to increment PC
- Sign and Zero **extender** for immediate constant
- **ALU** for executing instructions

Next . . .


- Designing a Processor: Step-by-Step
- Datapath Components and Clocking
- Assembling an Adequate Datapath
- Controlling the Execution of Instructions
- The Main Controller and ALU Controller
- Drawback of the single-cycle processor design



Components of the Datapath


■ Combinational Elements

 - ALU, Adder
- Immediate extender
- Multiplexers



■ Storage Elements

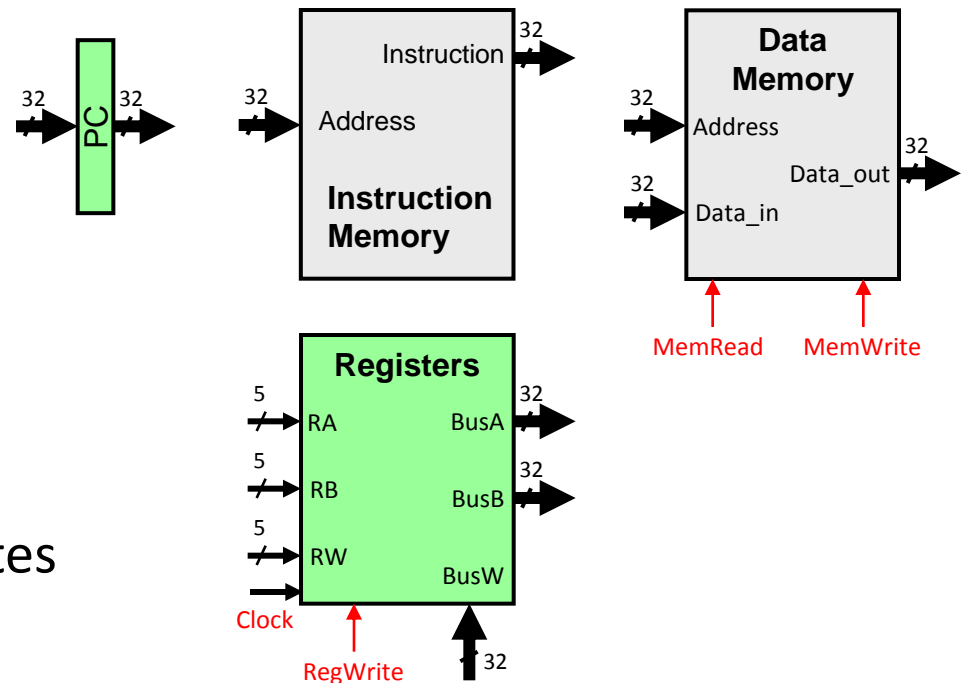- Instruction memory
- Data memory
- PC register
- Register file



■ Clocking methodology

- Timing of reads and writes

Register Element

- Register

- Similar to the D-type Flip-Flop


- n-bit input and output

- Write Enable:

- Enable / disable writing of register
 - Negated (0): Data_Out will not change
 - Asserted (1): Data_Out will become Data_In **after clock edge**


- Edge triggered Clocking

 - Register output is modified at **clock edge**





MIPS Register File

- Register File consists of 32×32 -bit registers
 - **BusA** and **BusB**: 32-bit output busses for reading 2 registers
 - **BusW**: 32-bit input bus for writing a register when **RegWrite** is 1
 - Two registers read and one written in a cycle
- Registers are selected by:
 - **RA** selects register to be **read** on **BusA**
 - **RB** selects register to be **read** on **BusB**
 - **RW** selects the register to be **written**
- Clock input
 - The clock input is **used ONLY during write** operation
 - During read, register file behaves as a **combinational logic** block
 - RA or RB valid => BusA or BusB valid after **access time**

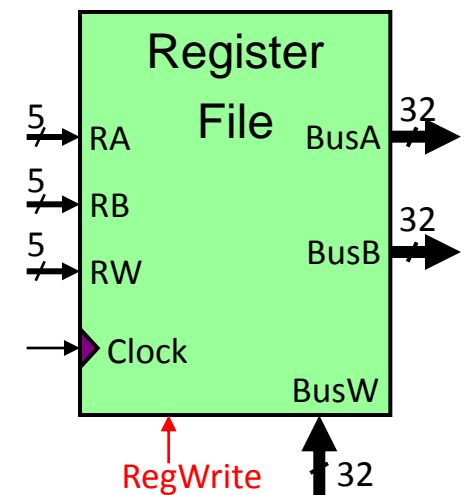


Tri-State Buffers

  - Allow multiple sources to drive a single bus
- Two Inputs:
 - Data signal (data_in)
 - Output enable
- One Output (data_out):
 - If (Enable) Data_out = Data_in
 - else Data_out = High Impedance state (output is disconnected)
- Tri-state buffers can be used to build multiplexors







Building a Multifunction ALU

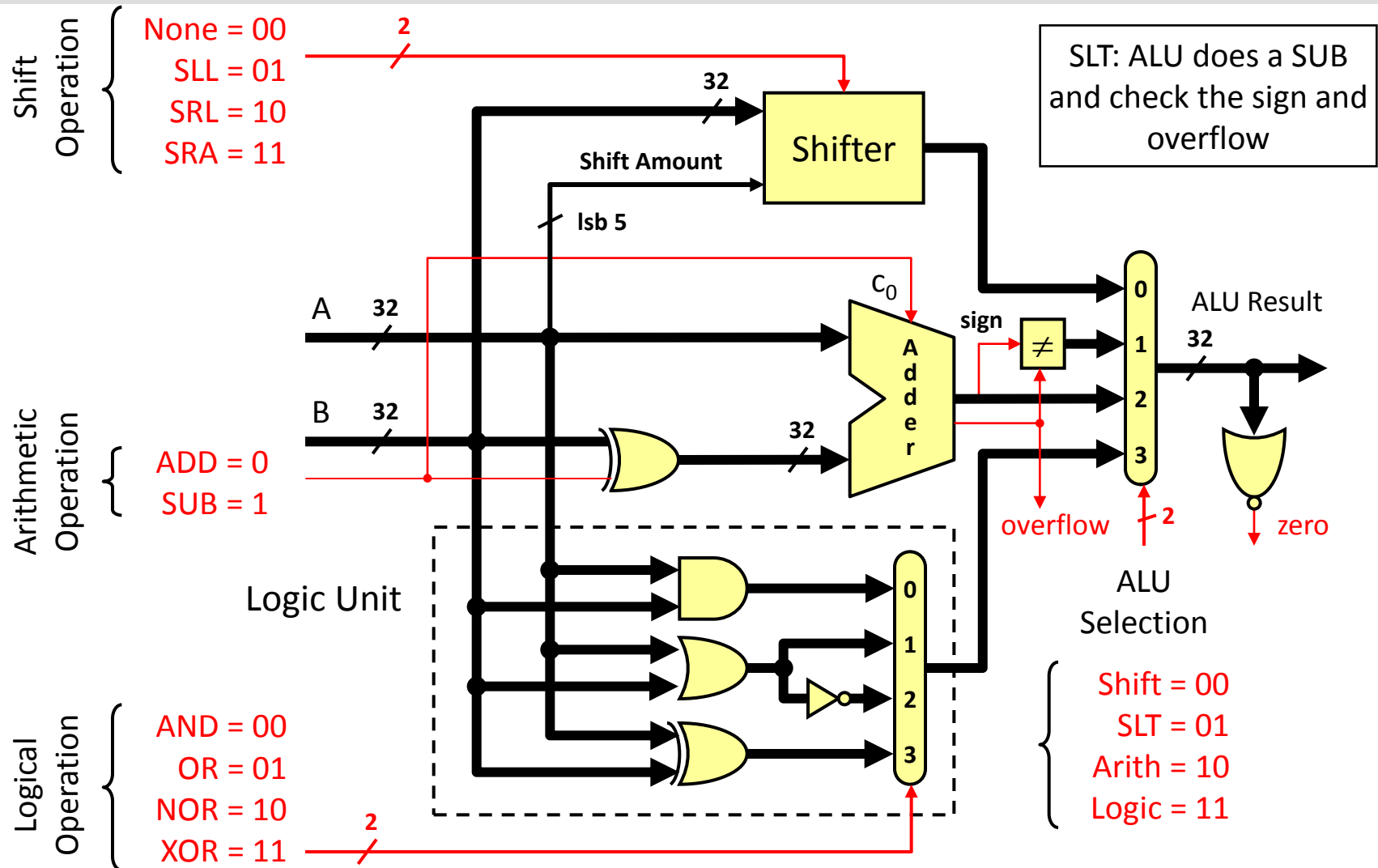


Instruction and Data Memories

- Instruction memory needs only provide read access
 - Because datapath does not write instructions
 - Behaves as combinational logic for read
 - **Address** selects **Instruction** after **access time**
- Data Memory is used for load and store
 - **MemRead**: enables output on **Data_out**
 - **Address** selects the word to put on **Data_out**
 - **MemWrite**: enables writing of **Data_in**
 - **Address** selects the memory word to be written
 - The **Clock** synchronizes the write operation
- Separate instruction and data memories
 - Later, we will replace them with **caches**

  


Clocking Methodology

- Clocks are needed in a sequential logic to decide when a state element (register) should be updated
- To ensure correctness, a **clocking methodology** defines when data can be written and read
- We assume **edge-triggered clocking**
- All state changes occur on the **same clock edge**
- Data must be **valid** and **stable** before arrival of clock edge
- Edge-triggered clocking allows a register to be read and written during same clock cycle

 

Determining the Clock Cycle

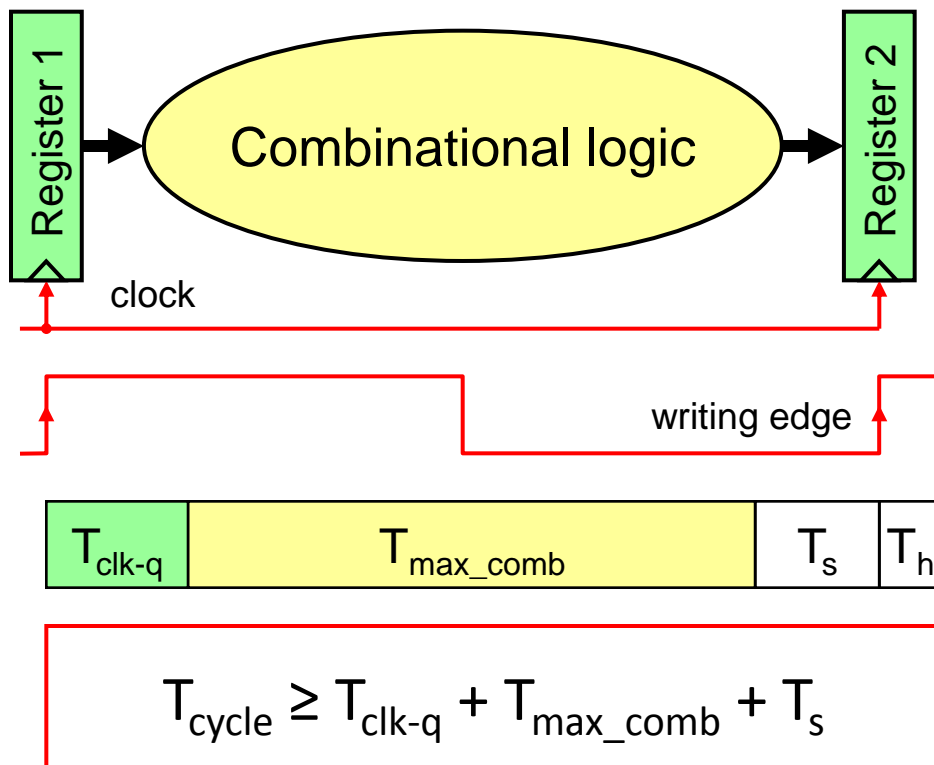- With edge-triggered clocking, the clock cycle must be long enough to accommodate the path from one register through the combinational logic to another register



- $T_{\text{clk-q}}$: clock to output delay through register
- $T_{\text{max_comb}}$: longest delay through combinational logic
- T_s : setup time that input to a register must be stable before arrival of clock edge
- T_h : hold time that input to a register must hold after arrival of clock edge
- Hold time (T_h) is normally satisfied since $T_{\text{clk-q}} > T_h$

Clock Skew

- Clock skew arises because the clock signal uses different paths with slightly different delays to reach state elements
- Clock skew is the difference in absolute time between when two storage elements see a clock edge
- With a clock skew, the clock cycle time is increased

$$T_{\text{cycle}} \geq T_{\text{clk-q}} + T_{\text{max_combinational}} + T_{\text{setup}} + T_{\text{skew}}$$

- Clock skew is reduced by balancing the clock delays


Next . . .

- Designing a Processor: Step-by-Step
- Datapath Components and Clocking
- Assembling an Adequate Datapath
- Controlling the Execution of Instructions
- The Main Controller and ALU Controller
- Drawback of the single-cycle processor design



Instruction Fetching Datapath

 
- We can now assemble the datapath from its components
- For instruction fetching, we need ...
 - Program Counter (PC) register
 - Instruction Memory
 - Adder for incrementing PC



The least significant 2 bits of the PC are '00' since PC is a multiple of 4


Datapath does not handle branch or jump instructions

 Improved datapath increments **upper 30 bits** of PC **by 1**




Improved Datapath

Datapath for R-type Instructions

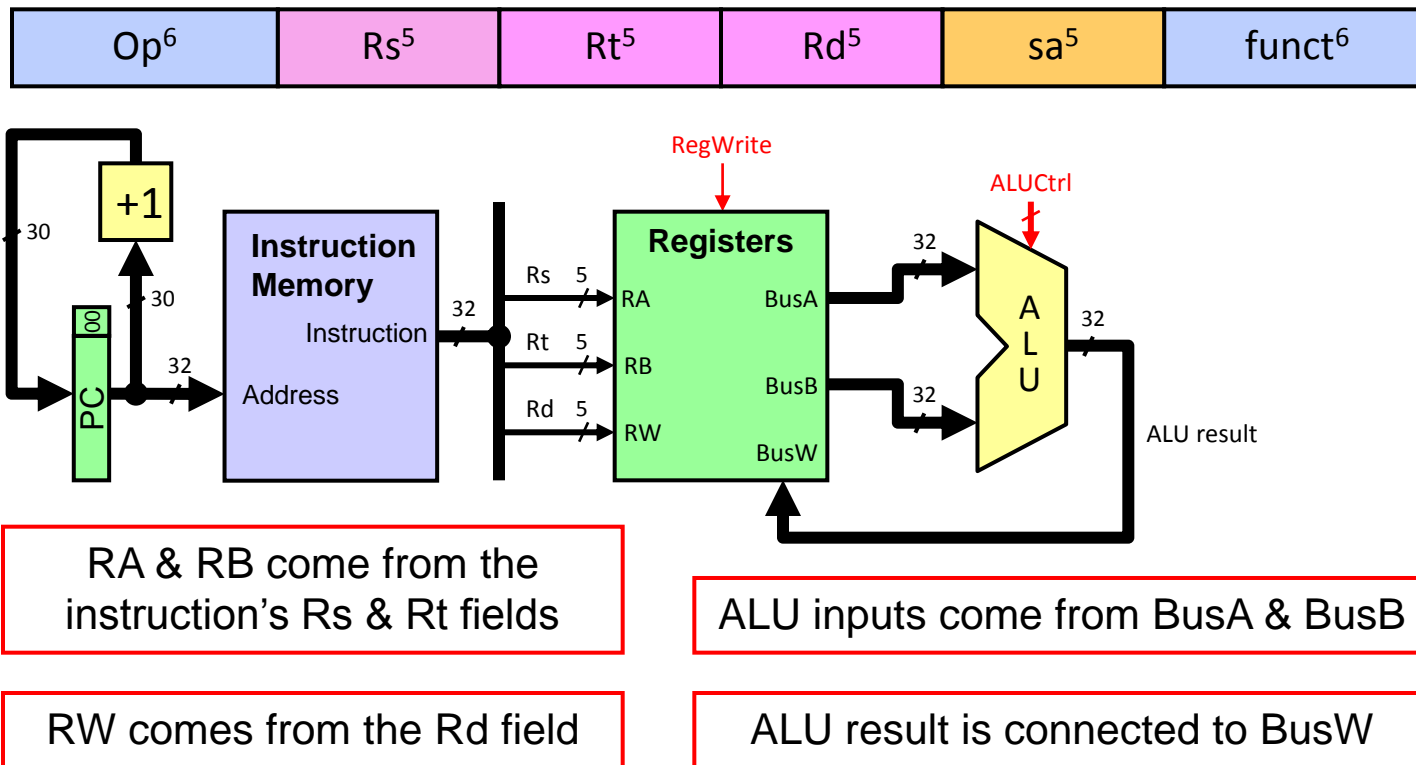

■ Control signals

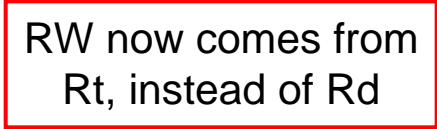- $ALU Ctrl$ is derived from the $funct$ field because $Op = 0$ for R-type
- $RegWrite$ is used to enable the writing of the ALU result




Second ALU input comes from the extended immediate

RB and BusB are not used

- RB and BusB are not used

Combining R-type & I-type Datapaths

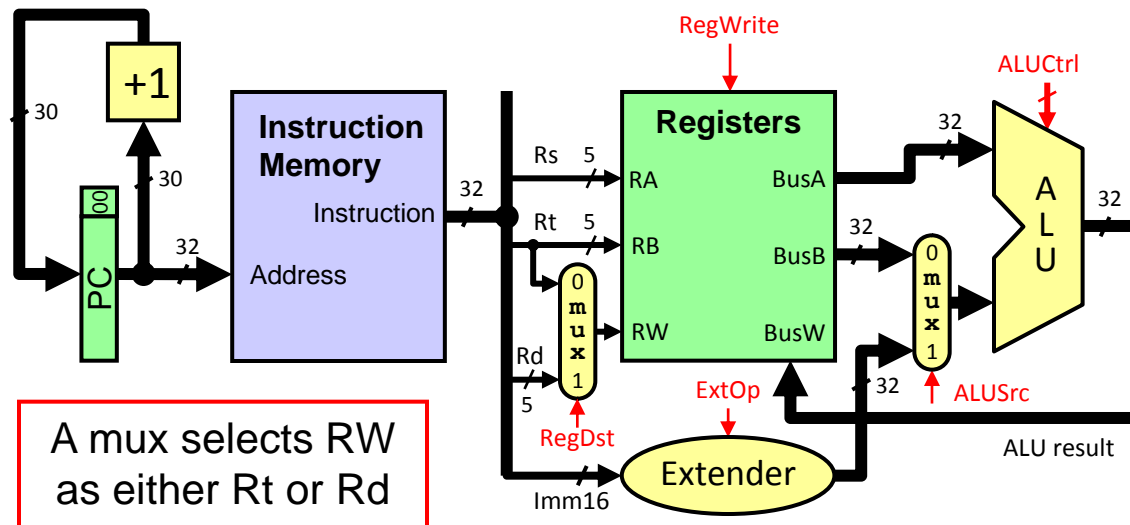


Another mux selects 2nd ALU input as either source register Rt data on BusB or the extended immediate


■ Control signals

- **ALU Ctrl** is derived from either the **Op** or the **funct** field
- **RegWrite** enables the writing of the **ALU result**
- **ExtOp** controls the extension of the 16-bit immediate
- **RegDst** selects the register destination as either **Rt** or **Rd**
- **ALUSrc** selects the 2nd ALU source as **BusB** or **extended immediate**

Controlling ALU Instructions

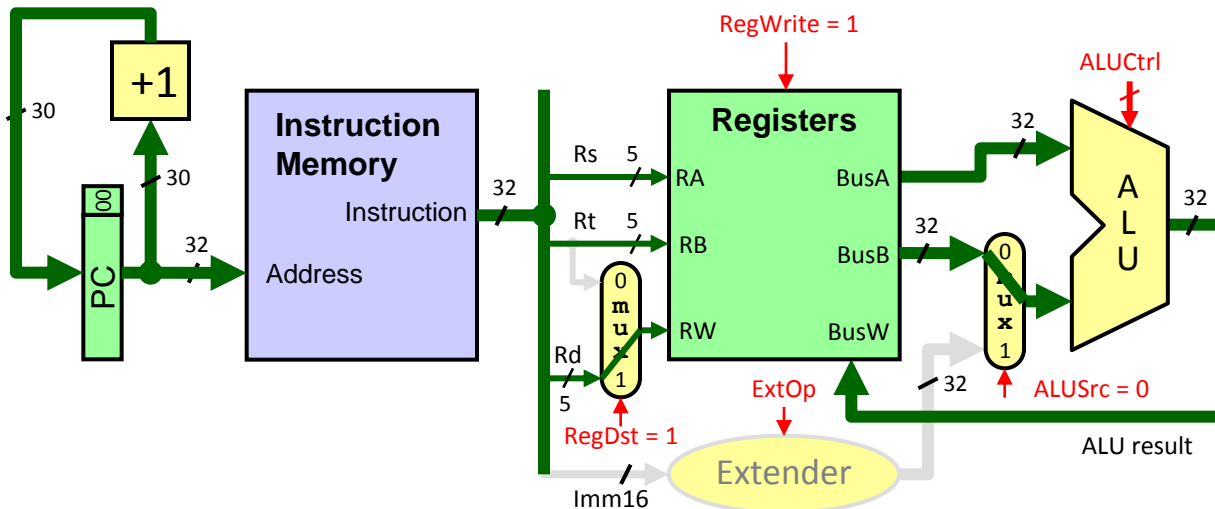


For R-type ALU instructions, **RegDst** is '1' to select Rd on RW and **ALUSrc** is '0' to select BusB as second ALU input. The active part of datapath is shown in **green**

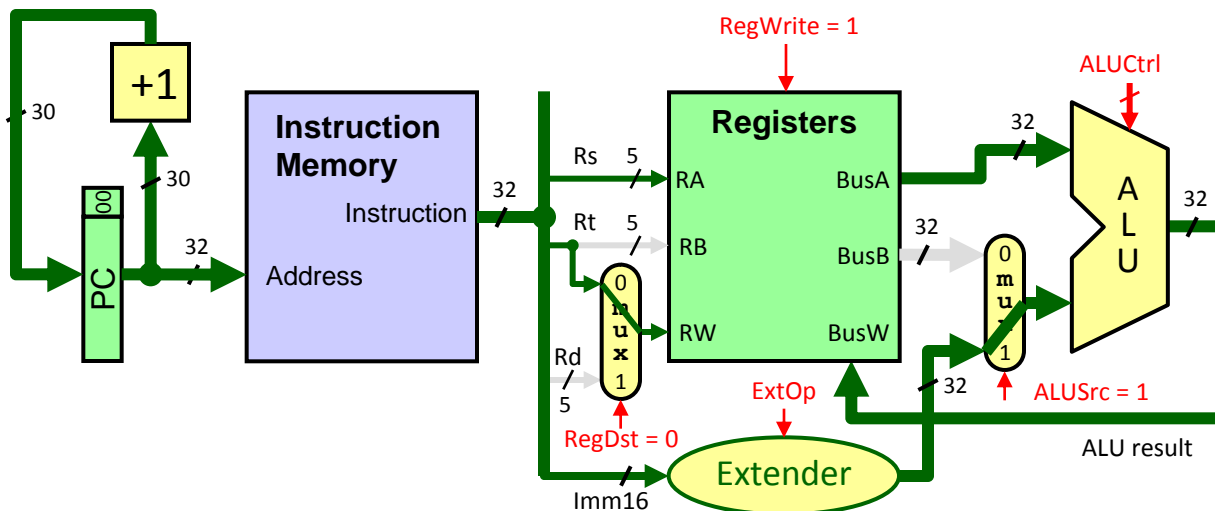

For I-type ALU instructions, **RegDst** is '0' to select Rt on RW and **ALUSrc** is '1' to select Extended immediate as second ALU input. The active part of datapath is shown in **green**


Details of the Extender

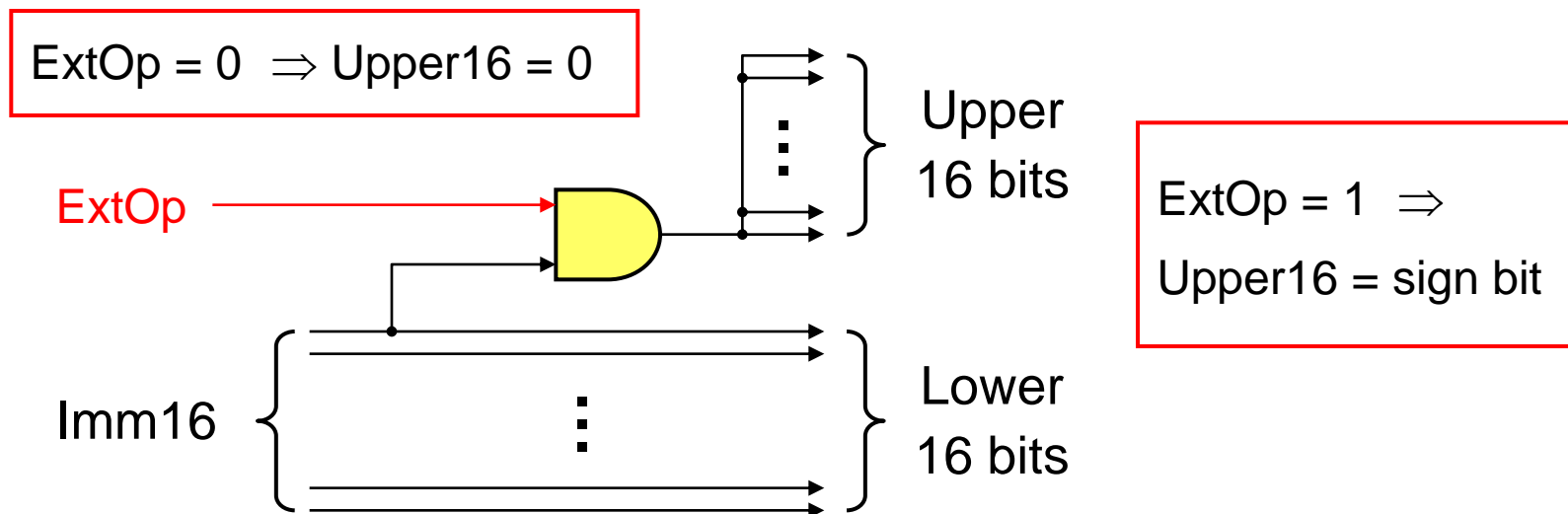- Two types of extensions
 - Zero-extension for unsigned constants
 - Sign-extension for signed constants
- Control signal **ExtOp** indicates type of extension
- Extender Implementation: wiring and one AND gate



Adding Data Memory to Datapath

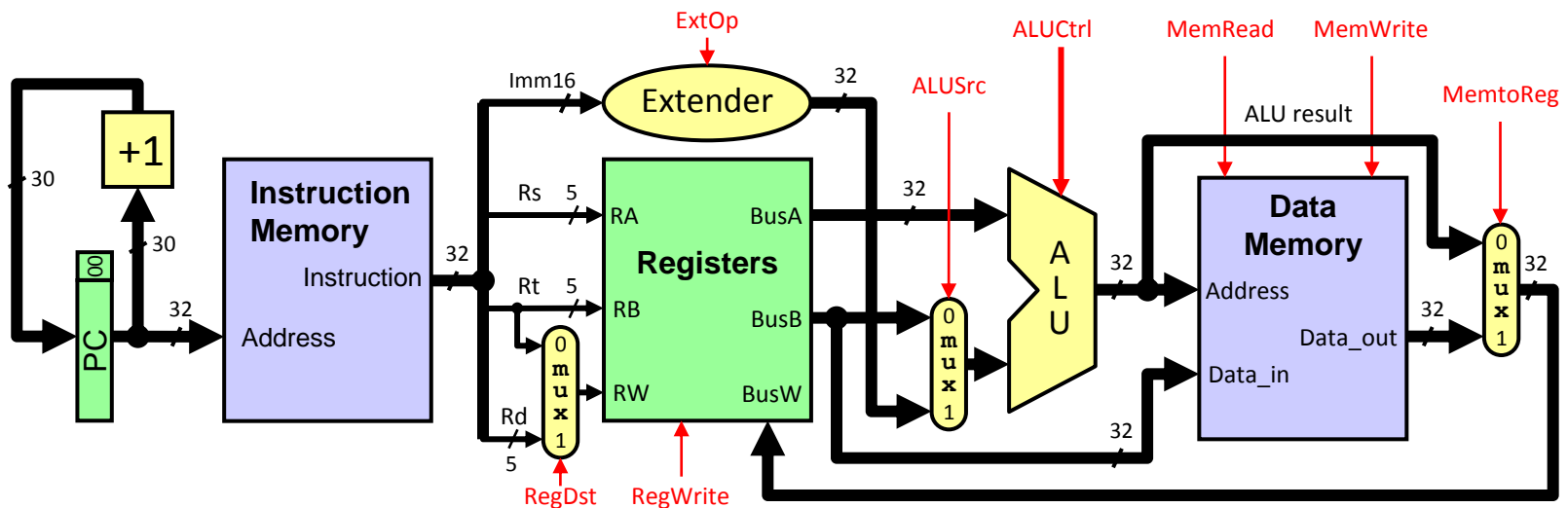- A **data memory** is added for **load** and **store** instructions



ALU calculates data memory address


A 3rd mux selects data on BusW as either ALU result or memory data_out

Additional Control signals

- **MemRead** for load instructions
- **MemWrite** for store instructions
- **MemtoReg** selects data on BusW as **ALU result** or **Memory Data_out**


BusB is connected to Data_in of Data Memory for store instructions

Controlling the Execution of Load

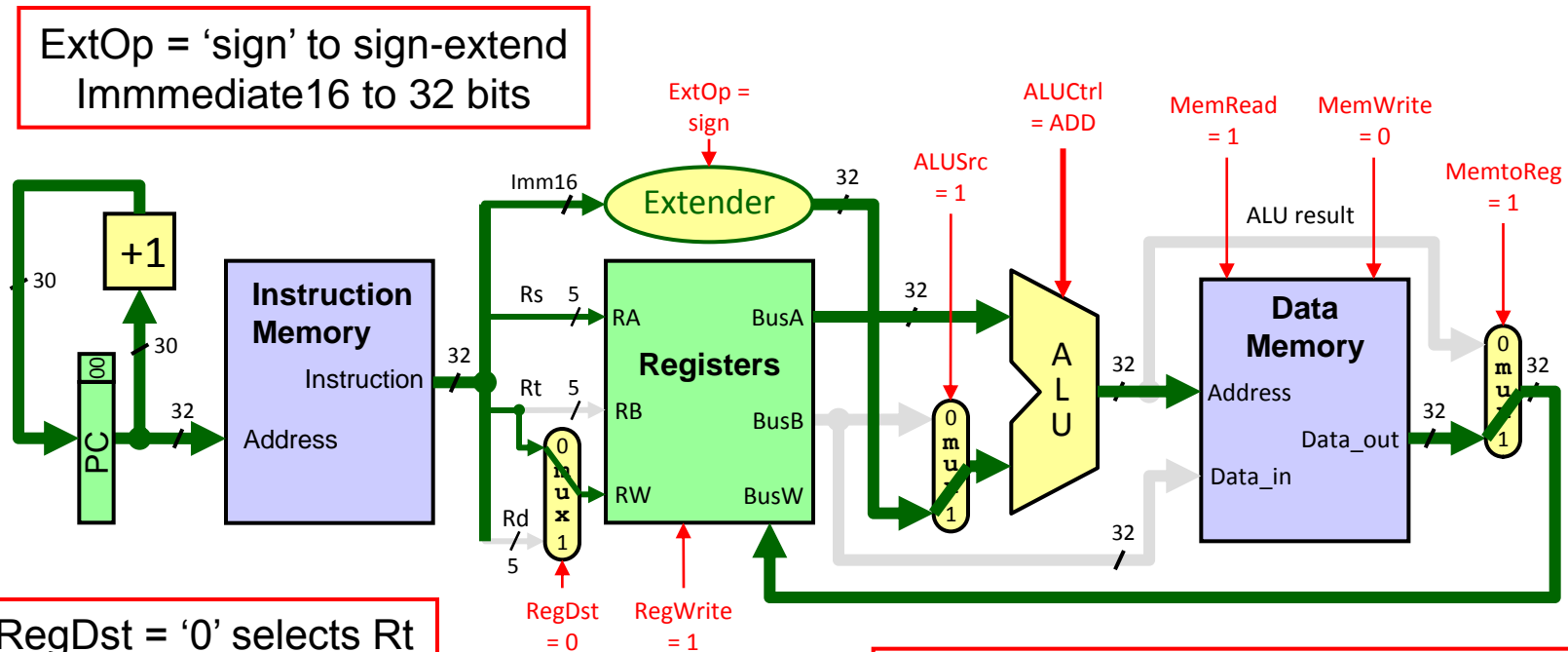

Controlling the Execution of Store

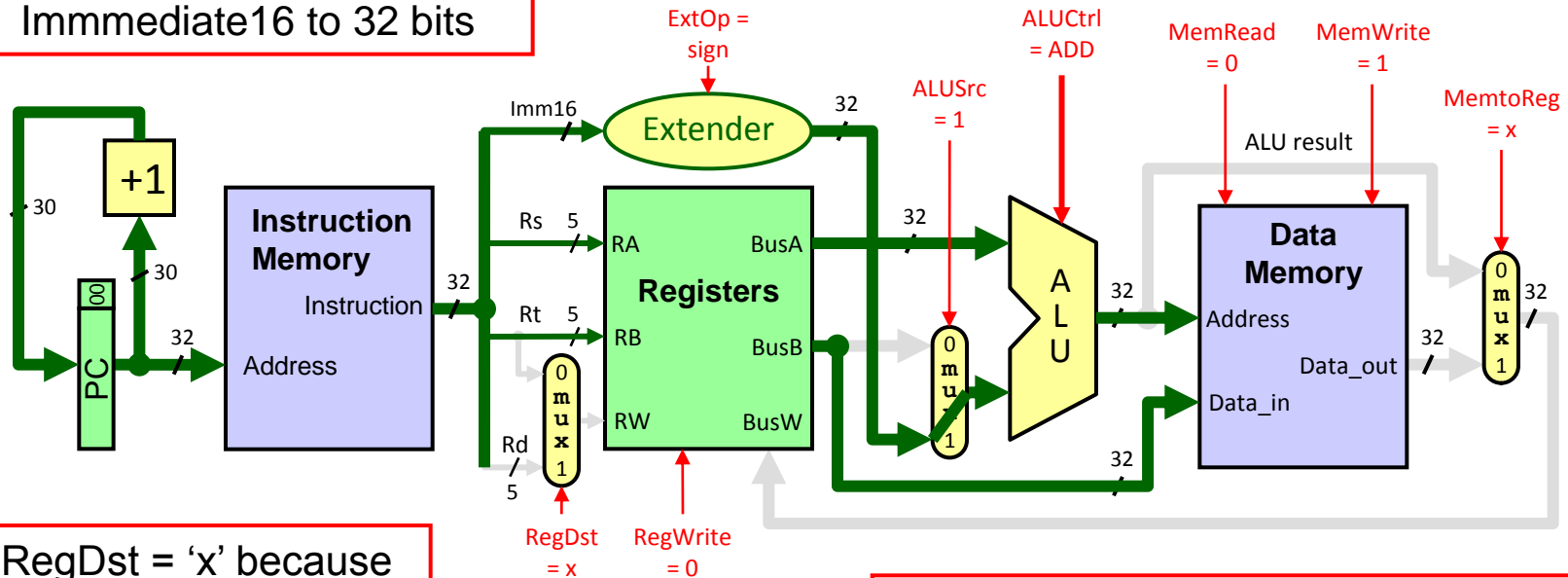ExtOp = 'sign' to sign-extend
Immediate16 to 32 bits



RegDst = 'x' because
no destination register

ALUSrc = '1' to select the extended
immediate as second ALU input


ALUCtrl = 'ADD' to calculate data memory
address as $\text{Reg}(\text{Rs}) + \text{sign-extend}(\text{Imm16})$

MemWrite = '1' to write data memory

MemtoReg = 'x' because we don't
care what data is placed on BusW

RegWrite = '0' because no register is
written by the store instruction

Adding Jump and Branch to Datapath

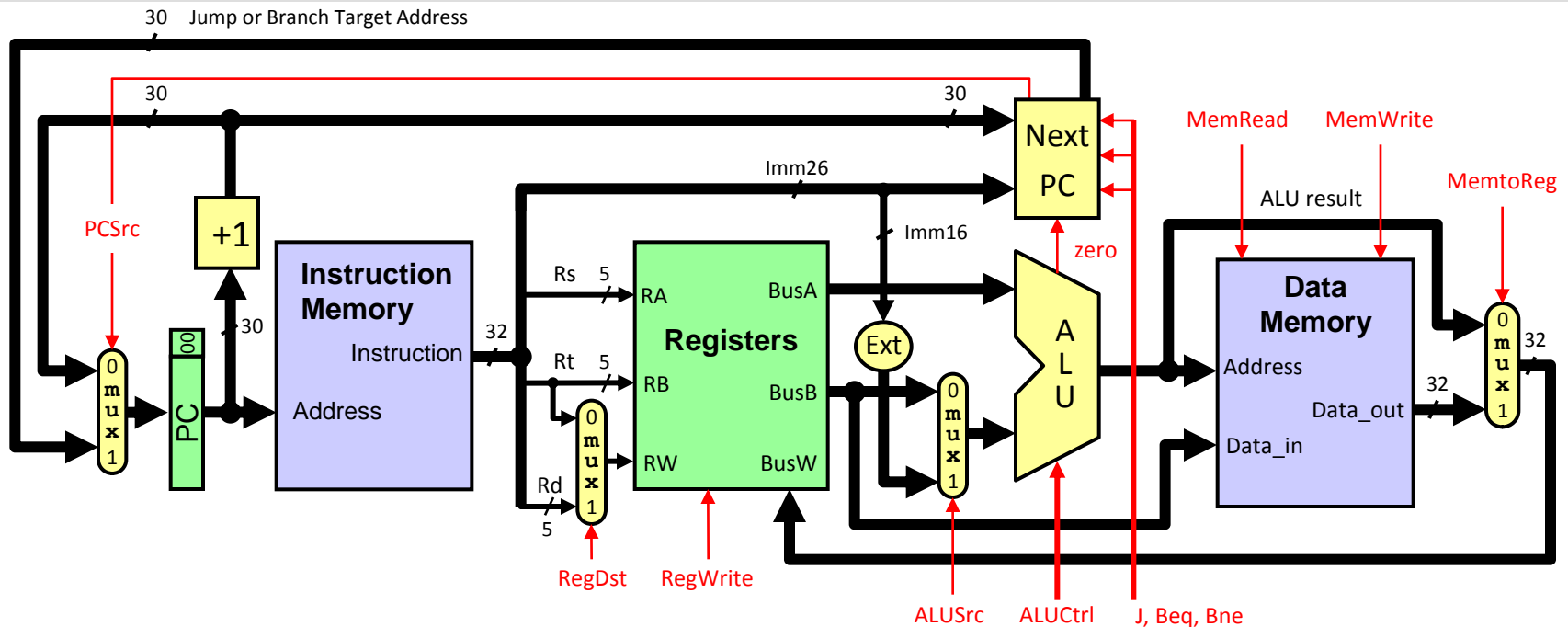


- Additional Control Signals
 - J, Beq, Bne for jump and branch instructions
 - Zero condition of the ALU is examined
 - PCSrc = 1 for Jump & taken Branch

Next PC computes jump or branch target instruction address

For Branch, ALU does a subtraction

Details of Next PC

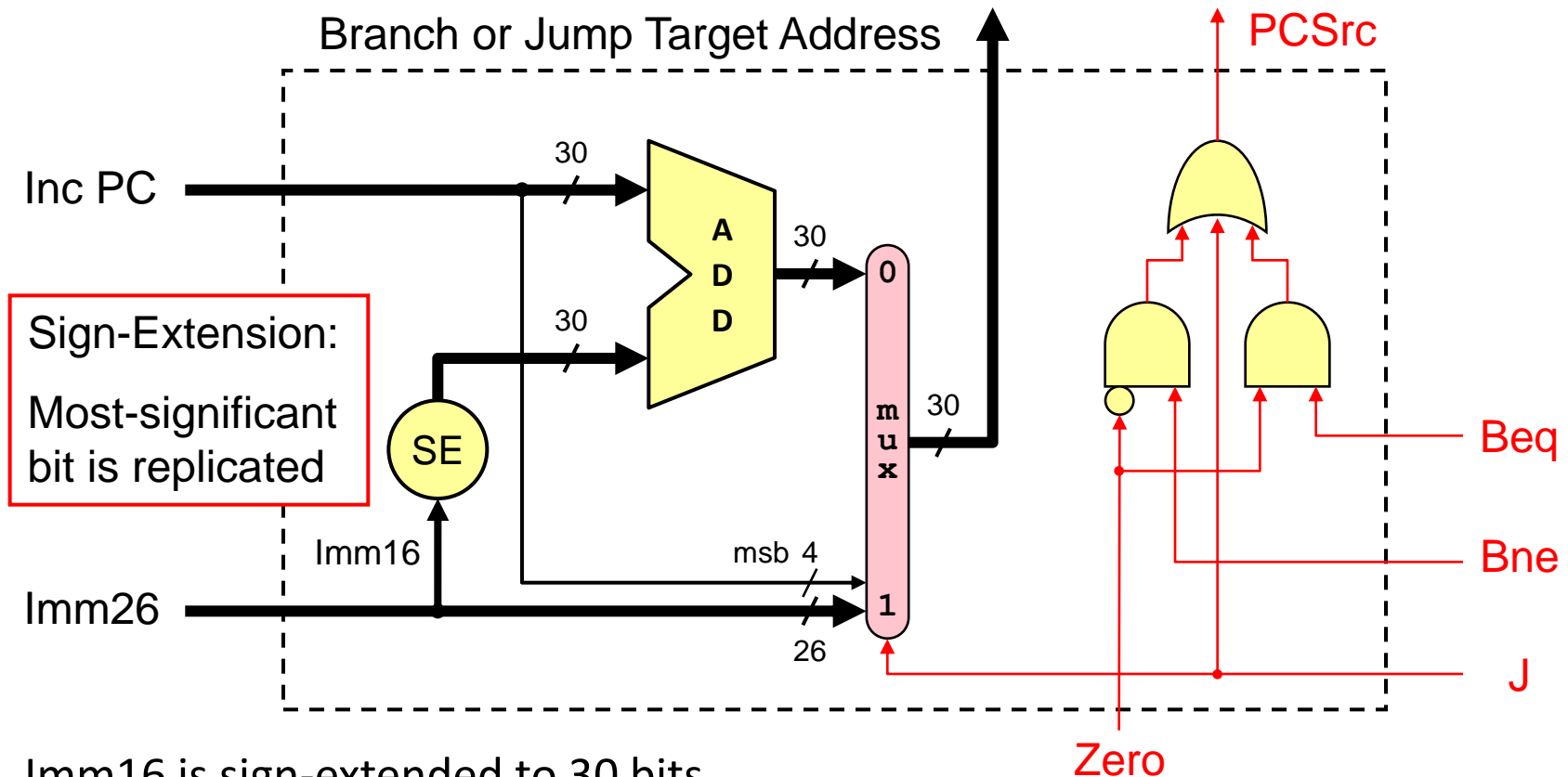


Imm16 is sign-extended to 30 bits

Jump target address: upper 4 bits of PC are concatenated with Imm26

$$PCSrc = J + (Beq \cdot Zero) + (Bne \cdot Zero)$$

Controlling the Execution of Jump

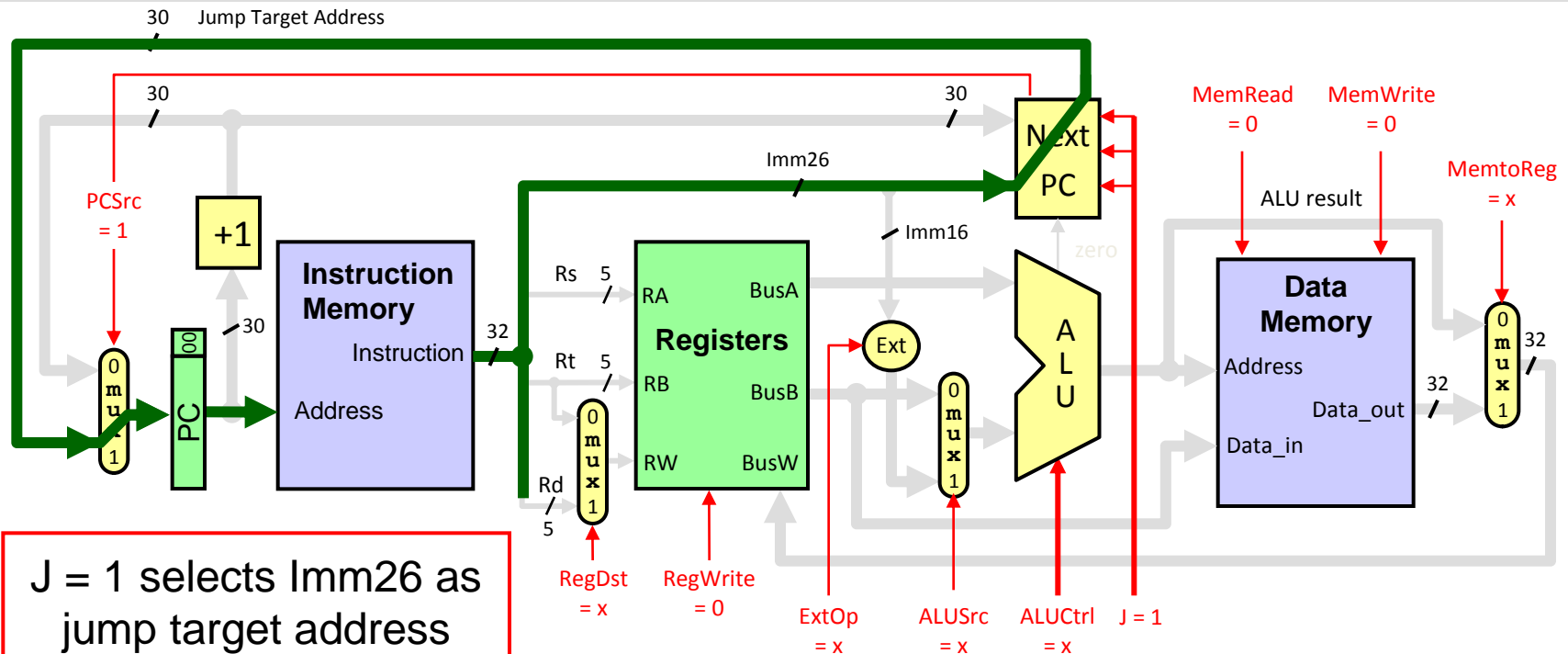

J = 1 selects Imm26 as jump target address


Upper 4 bits are from the incremented PC

$PCSrc = 1$ to select jump target address

MemRead, MemWrite & RegWrite are 0

We don't care about RegDst, ExtOp, ALUSrc, ALUCtrl, and MemtoReg

Controlling the Execution of Branch

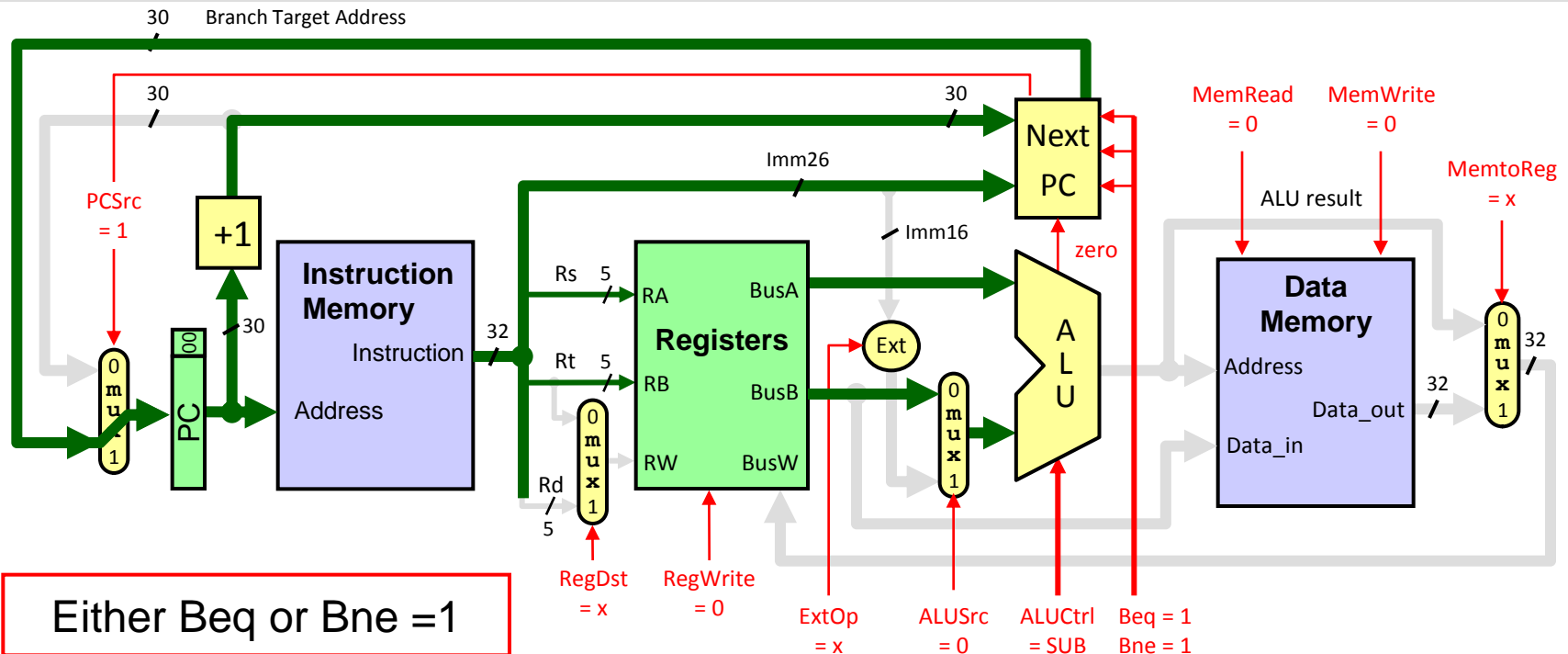

Either Beq or Bne = 1

Next PC outputs branch target address

ALUSrc = '0' (2nd ALU input is BusB)
ALUctrl = 'SUB' produces zero flag

Next PC logic determines PCSrc according to zero flag

MemRead = MemWrite = RegWrite = 0


RegDst = ExtOp = MemtoReg = x

Next . . .

- Designing a Processor: Step-by-Step
- Datapath Components and Clocking
- Assembling an Adequate Datapath
- Controlling the Execution of Instructions
- The Main Controller and ALU Controller
- Drawback of the single-cycle processor design



Main Control and ALU Control

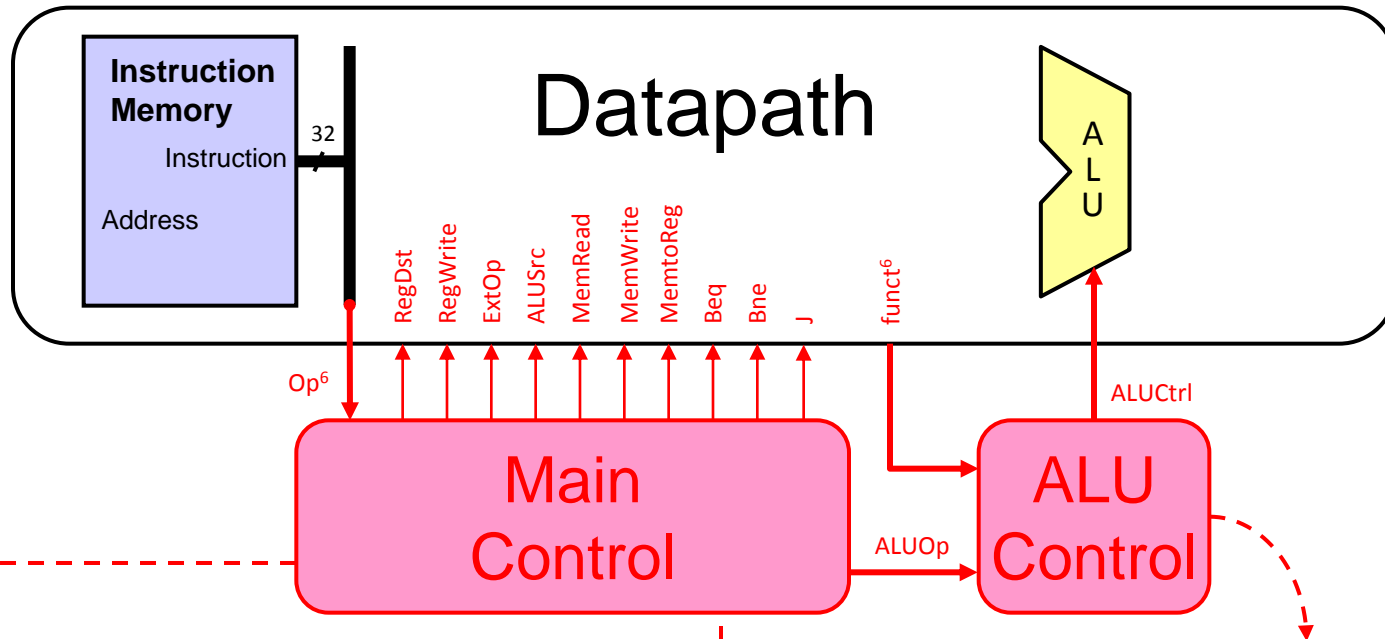

Input:

- 6-bit **opcode** field from instruction

Output:

- 10 **control signals** for datapath
- **ALUOp** for ALU Control


Input:

- ✧ 6-bit **function** field from instruction
- ✧ **ALUOp** from main control

Output:

- ✧ **ALUCtrl** signal for ALU

Single-Cycle Datapath + Control

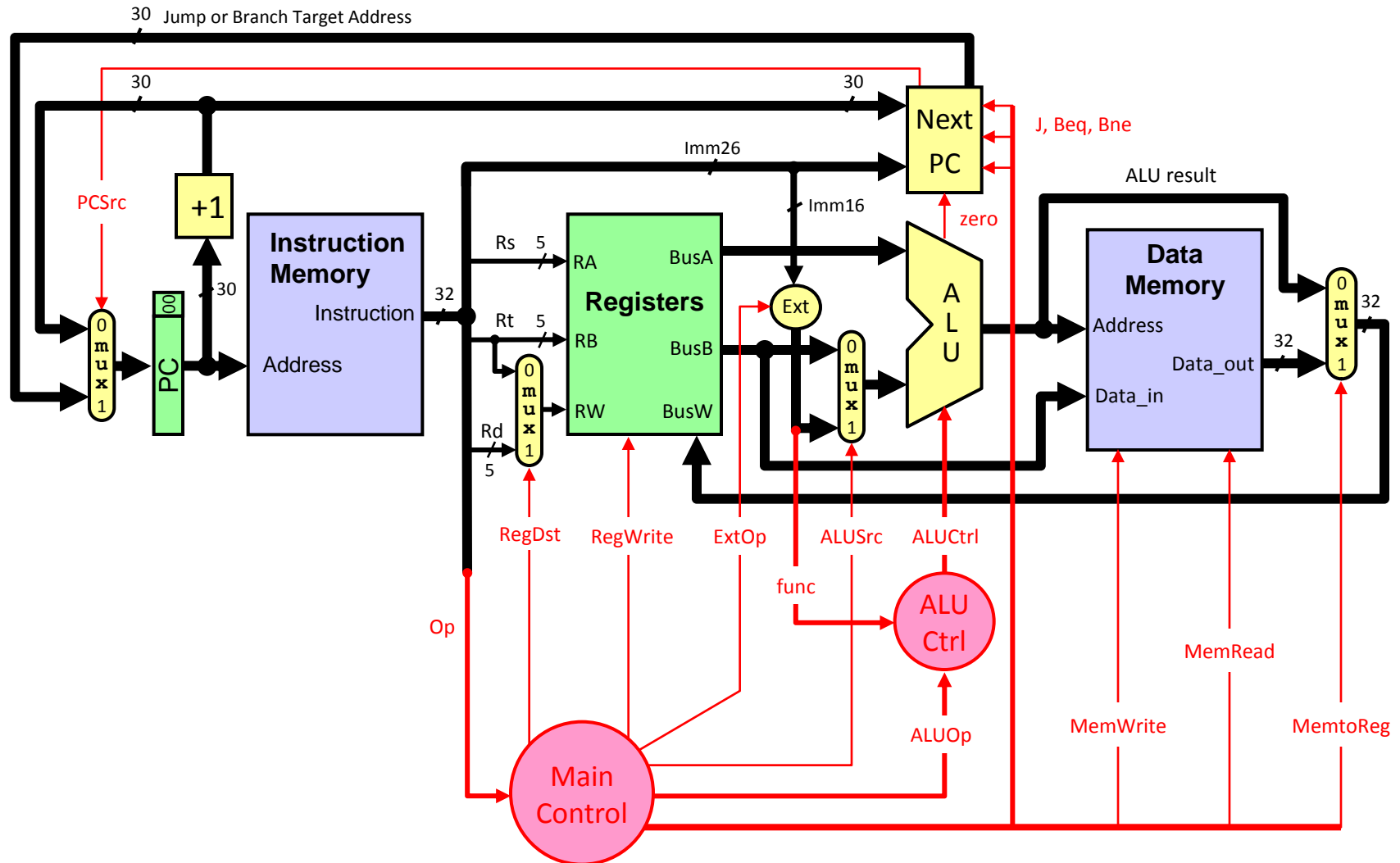

Main Control Signals

Signal	Effect when '0'	Effect when '1'
RegDst	Destination register = Rt	Destination register = Rd
RegWrite	None	Destination register is written with the data value on BusW
ExtOp	16-bit immediate is zero-extended	16-bit immediate is sign-extended
ALUSrc	Second ALU operand comes from the second register file output (BusB)	Second ALU operand comes from the extended 16-bit immediate
MemRead	None	Data memory is read $\text{Data_out} \leftarrow \text{Memory}[\text{address}]$
MemWrite	None	Data memory is written $\text{Memory}[\text{address}] \leftarrow \text{Data_in}$
MemtoReg	BusW = ALU result	BusW = Data_out from Memory
Beq, Bne	$\text{PC} \leftarrow \text{PC} + 4$	$\text{PC} \leftarrow \text{Branch target address}$ If branch is taken
J	$\text{PC} \leftarrow \text{PC} + 4$	$\text{PC} \leftarrow \text{Jump target address}$
ALUOp	This multi-bit signal specifies the ALU operation as a function of the opcode	



Main Control Signal Values

Op	Reg Dst	Reg Write	Ext Op	ALU Src	ALU Op	Beq	Bne	J	Mem Read	Mem Write	Mem toReg
R-type	1 = Rd	1	x	0=BusB	R-type	0	0	0	0	0	0
addi	0 = Rt	1	1=sign	1=Imm	ADD	0	0	0	0	0	0
slti	0 = Rt	1	1=sign	1=Imm	SLT	0	0	0	0	0	0
andi	0 = Rt	1	0=zero	1=Imm	AND	0	0	0	0	0	0
ori	0 = Rt	1	0=zero	1=Imm	OR	0	0	0	0	0	0
xori	0 = Rt	1	0=zero	1=Imm	XOR	0	0	0	0	0	0
lw	0 = Rt	1	1=sign	1=Imm	ADD	0	0	0	1	0	1
sw	x	0	1=sign	1=Imm	ADD	0	0	0	0	1	x
beq	x	0	x	0=BusB	SUB	1	0	0	0	0	x
bne	x	0	x	0=BusB	SUB	0	1	0	0	0	x
j	x	0	x	x	x	0	0	1	0	0	x

■ X is a don't care (can be 0 or 1), used to minimize logic

Logic Equations for Control Signals

RegDst \leq R-type

RegWrite \leq (sw + beq + bne + j)


ExtOp \leq (andi + ori + xori)

ALUSrc \leq (R-type + beq + bne)

MemRead \leq lw

MemWrite \leq sw

MemtoReg \leq lw

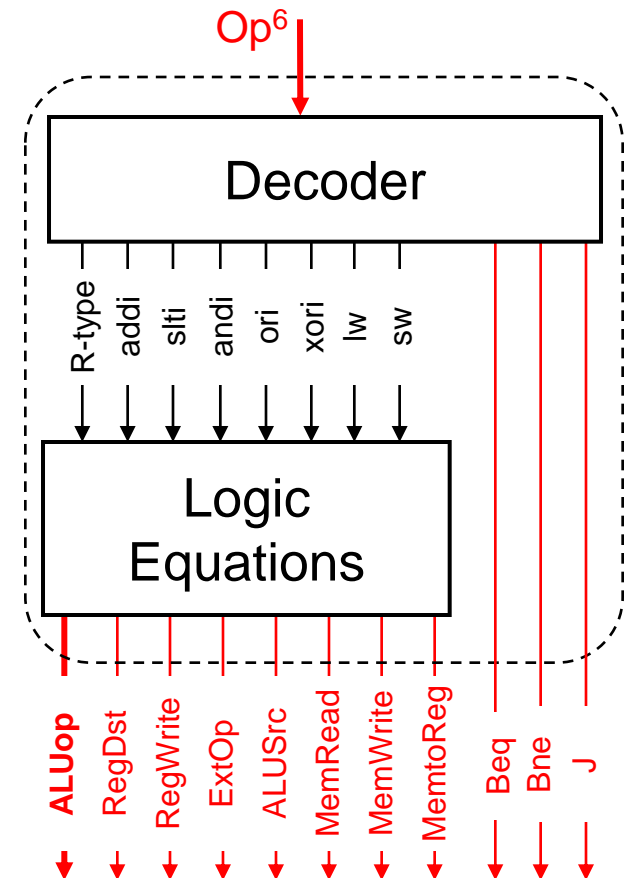

ALU Control Truth Table

Op ⁶	ALU Control			4-bit Encoding
	ALUOp	funct ⁶	ALUCtrl	
R-type	R-type	add	ADD	0000
R-type	R-type	sub	SUB	0010
R-type	R-type	and	AND	0100
R-type	R-type	or	OR	0101
R-type	R-type	xor	XOR	0110
R-type	R-type	slt	SLT	1010
addi	ADD	x	ADD	0000
slti	SLT	x	SLT	1010
andi	AND	x	AND	0100
ori	OR	x	OR	0101
xori	XOR	x	XOR	0110
lw	ADD	x	ADD	0000
sw	ADD	x	ADD	0000
beq	SUB	x	SUB	0010
bne	SUB	x	SUB	0010
j	x	x	x	x

The 4-bit encoding for ALUctrl is chosen here to be equal to the last 4 bits of the function field

Other binary encodings are also possible. The idea is to choose a binary encoding that will minimize the logic for ALU Control




Next . . .

- Designing a Processor: Step-by-Step
- Datapath Components and Clocking
- Assembling an Adequate Datapath
- Controlling the Execution of Instructions
- The Main Controller and ALU Controller
- Drawback of the single-cycle processor design



Drawbacks of Single Cycle Processor

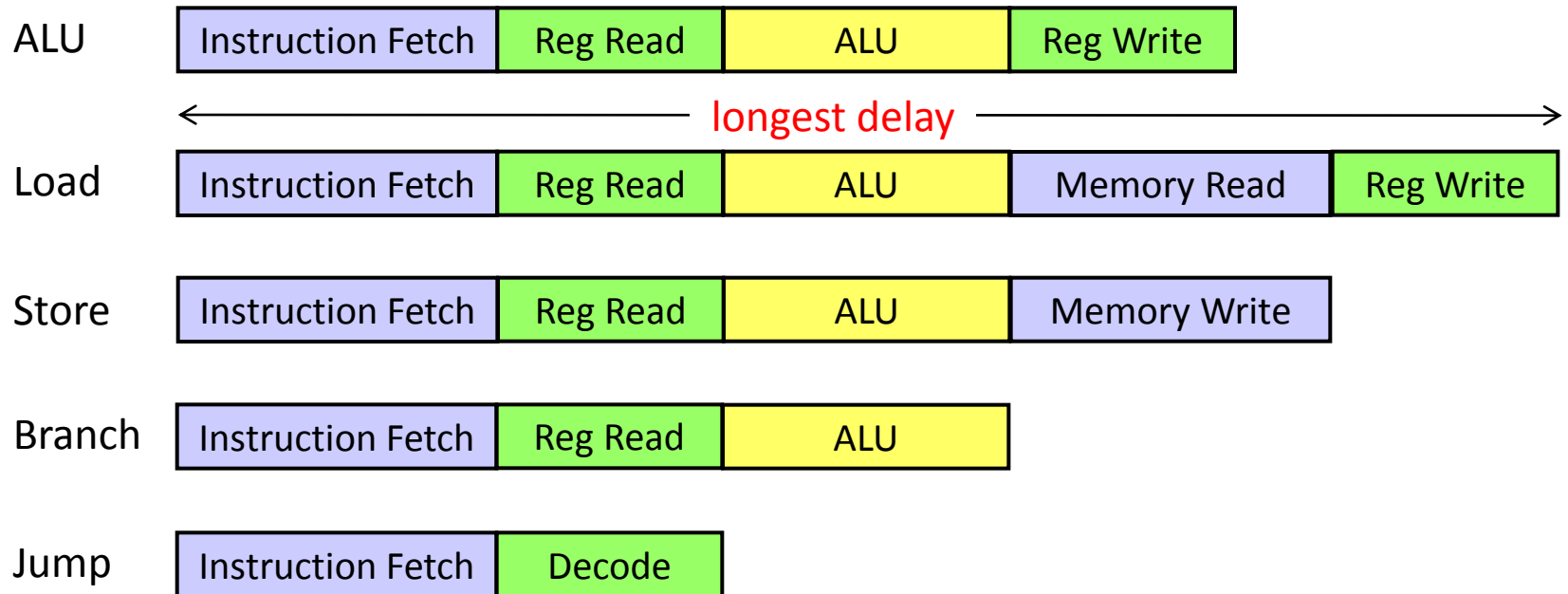- Long cycle time
 - All instructions take as much time as the **slowest**



- Alternative Solution: **Multicycle** implementation
 - Break down instruction execution into multiple cycles